

LDCO – ORAL Question Bank

Synchronous Counter

- Q.1) What do you mean by Synchronous Counter?
- Q.2) Differentiate Synchronous and Asynchronous counter.
- Q.3) Design and implement 2 bit Synchronous UP Counter using f/f.
- Q.4) Design and implement 2 bit Synchronous DOWN Counter using f/f.
- Q.5) Give Applications of counters.
- Q.6) Explain level triggered and edge triggered flip-flop.
- Q.7) State advantages of Synchronous Counter.
- Q.8) What is lock-out condition?
- Q.9) Compare Counters and Registers.
- Q.10) What is Decade counter?

Asynchronous Counter

- Q.1) What do you mean by Counter?
- Q.2) Which Flip-Flop's are normally used design a Counter & why?
- Q.3) What do you mean by Asynchronous Counter?
- Q.4) Explain MOD-N & MOD-NN Counter (IC 7490)
- Q.5) Explain internal diagram of 7490.
- Q.6) Why is input B connected to output QA.
- Q.7) Draw circuit diagram of 3 bit up & Down Asynchronous Counter using Flipflop.
- Q.8) What is glitch Problem?
- Q.9) Design MOD-6 using T Flip-Flop & 7490
- Q.10) Draw Connection diagram of 7493

Multiplexer

- Q.1) What is meant by Multiplexer?
- Q.2) What is meant by Tree?
- Q.3) Implement using 4:1 MUX $F(A, B) = \text{Summation}(0, 2)$
- Q.4) Implement using 4:1 MUX & 8:1 MUX $F(A, B, C) = \text{Summation}(0, 1, 5, 6)$
- Q.5) State Advantages of Multiplexer.
- Q.6) Give applications of Multiplexer.
- Q.7) Formula for finding No. of select lines in MUX is-----
- Q.8) ----- data lines are required for selecting 8 inputs.
- Q.9) ----- is also called as Selector.
- Q.10) MUX improves reliability of digital system because it -----no. of external wired connections.

DeMUX

- Q.1) Define Demux/Decoder.
- Q.2) What do you mean by Demultiplexer Tree?

- Q.3) Draw & Explain Logic diagram of Demultiplexer.
- Q.4) Implement 8 bit Comparator using Decoder.
- Q.5) Implement 3 bit odd & even parity generator using Decoder.
- Q.6) Differentiate MUX & DEMUX.
- Q.7) Demux has -----data input &-----output &-----select lines.
- Q.8) 1:4 Demux has -----input &-----output
- Q.9) -----circuit takes 1 input from source & distributes it to one of several output lines.
- Q.10) ----- is also called a Distributor.

BCD Adder

- Q.1) What is BCD code?
- Q.2) Compare BCD & Binary code?
- Q.3) Show BCD addition of a) $3+5$ b) $8+6$ c) $8+9$
- Q.4) Explain how EX-OR gate is used to design 1's complement circuit.
- Q.5) Give applications of BCD & Binary code.
- Q.6) For converting invalid BCD to valid BCD-----is added to it
- Q.7) Convert following to BCD,Binary,Excess-3 & Gray code.
a) 37 b) 18
- Q.8) Draw the circuit for 9's Complementor.
- Q.9) Draw circuit of BCD Subtractor.
- Q.10) Which IC's are needed to design BCD Subtractor.